

**Electrical Analogs  
for  
Knowles Electronics, LLC. Transducers  
Version 9.0**

by  
J. L. LoPresti

Knowles Electronics, Inc.  
1151 Maplewood Drive  
Itasca, IL 60143

# Contents

I.	Introduction.....	1
II.	Circuit Topology and Components.....	1
	Microphone Analog.....	1
	Receiver Analog.....	2
III	Netlist Modules and Subcircuits.....	3
	Node Numbering, Device Specifications, & Modules.....	3
	Receiver Modules, Node Numbers & Subcircuits.....	4
	Microphone Modules, Node Numbers, & Subcircuits.....	5
	Circuit Components, Tubes, and Coupler Cavities.....	5
IV.	Schematics Capture Libraries.....	6
	Receivers.....	6
	Microphones.....	6
V.	Acoustic Transmission Tubes.....	6
VI.	Helpful Hints & Troubleshooting.....	7
	Converting Analogs to Subcircuits for Other Programs.....	7
	Converting CGS to SI Units.....	8
	Micro-Cap Circuit Simulator.....	8
	Transient Analysis & CMAG Component.....	9
	References.....	9
	Acknowledgments & Comments.....	9
	Appendix A.	
	Catalog of Available Transducer Analogs.....	10
	Appendix B.	
	List of Special Components.....	20
	Appendix C.	
	Add Knowles Libraries to Orcad Schematics and Capture Parts Browser..	21
	Appendix D.	
	Noise Simulations with Microphone Analogs.....	24
	Appendix E.	
	Acoustical and Mechanical Analogs and Units.....	26
	Appendix F.	
	Netlist Modules and Library Subcircuits.....	27

## **LIMITED LICENSE AND DISCLAIMER**

Knowles Electronics, LLC (“Knowles”) offers a limited non-exclusive, non-transferable license to access and use to its file of electrical circuit analogs of miniature transducer products (the “Files”) free of charge as an accommodation to you, the user, upon and subject to the following conditions, limitations and disclaimers. ANY INITIAL OR CONTINUED ACCESS TO, OR USE OF, THE FILES SHALL EVIDENCE AND CONFIRM YOUR UNDERSTANDING AND AGREEMENT TO THE FOLLOWING CONDITIONS AND LIMITATIONS.

1. **User Acknowledgements Regarding the Files.** You, the user of the Files, agree and acknowledge that access to the Files is provided AS IS AND WITHOUT WARRANTIES, EXPRESSED OR IMPLIED, INCLUDING IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE AND WARRANTIES AS TO ACCURACY, COMPLETENESS OR SUITABILITY FOR ANY PURPOSE. You agree to not rely on the Files or any information or data contained in the Files without independent verification and it is your responsibility to verify all data and information contained in the Files before relying upon it. Knowles expressly disclaims any liability for errors or omissions in the Files or any information or data contained in the Files, or your use of, reliance upon or interpretation of such information or data. Nothing contained in the Files shall be construed as, or be referenced as evidencing expansion, modification or interpretation of any product warranty or any agreement between you and Knowles.

2. **Ownership.** You understand and acknowledge that (i) the Files may include proprietary or confidential information; (ii) the Files, including all copyrights and other intellectual property rights are owned by Knowles; and (iii) you will do nothing to impair or interfere with any such rights of Knowles.

3. **Liability.** IN NO EVENT SHALL KNOWLES, OR ANY OF ITS PARENT, SUBSIDIARY OR AFFILIATED ENTITIES, OR ANY OF ITS OFFICERS, DIRECTORS OR EMPLOYEES, BE LIABLE TO YOU FOR ANY DAMAGES WHATSOEVER (INCLUDING, WITHOUT LIMITATION, DAMAGES FOR LOSS OF PROFITS, BUSINESS INTERRUPTION, LOSS OF BUSINESS INFORMATION OR OTHER LOSS OR DAMAGE) ARISING OUT OF YOUR USE OF, OR INABILITY TO USE, ANY OF THE FILES.

# ELECTRICAL ANALOGS FOR KNOWLES ELECTRONICS TRANSDUCERS

## I. Introduction

Acoustical and mechanical systems have resistive and reactive elements that behave like their electrical counterparts. These elements can be replaced by their analogs to build a circuit model that will simulate the response of a transducer. The Knowles analogs break down microphones and receivers into equivalent circuits for PSpice simulations. This report gives an overview of the transducer analog circuits and components. There is detailed information on node numbering and device specification for linking these files to your own models.

## II. Circuit Topology and Components

### Microphone Analog

The microphone analog is represented schematically in Fig. 1. The electret motor converts acoustic energy (pressure, volume velocity) into mechanical energy (force, velocity) and mechanical energy (force, velocity) into electrical energy (voltage and current).

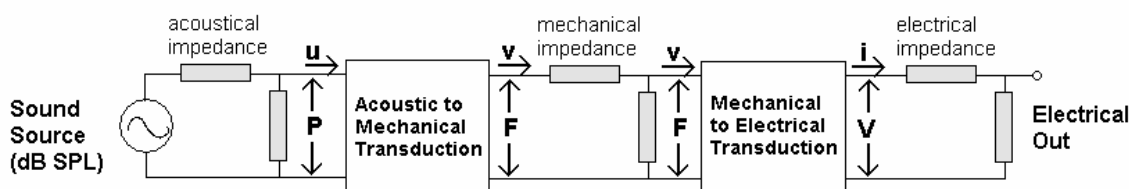


FIG. 1: Acoustical  $\Leftrightarrow$  mechanical  $\Leftrightarrow$  electrical transduction of a microphone.

The circuit representing a Knowles microphone is shown in Fig. 2a. On the acoustic side of the transformer (i.e., to the left), voltage corresponds to the pressure in the microphone. In cgs units, we define 1 volt to be equivalent to 74 dB SPL (i.e., in SI / MKS units 0.1 volt equivalent to 74 dB SPL or 0.1 Pa). Starting at the port tube, there is a small moving mass of air (i.e., inductance) represented by an inductor (see Figure 2b on next page). The tube has a damping screen with a large acoustic resistance that is in series with the port inductance. At the end of the tube is the opening into the main body of the microphone. The enclosed front volume is subject to compression and can be represented by a capacitor. All sides of the cavity except one side are solid and the sound pressure can act no further. Therefore one side of the capacitor is connected to ground. On the remaining side of the cavity is the diaphragm and beyond the diaphragm is the rear volume shown as another capacitor. Other components have been combined to reduce the size of the circuit and are labeled "lump parameters". Since the circuit components are combined there is no longer a one to one correspondence to the parts in the microphone. Most module files and subcircuit definitions use the same circuit topology, component names, and node numbers shown in Fig. 2.


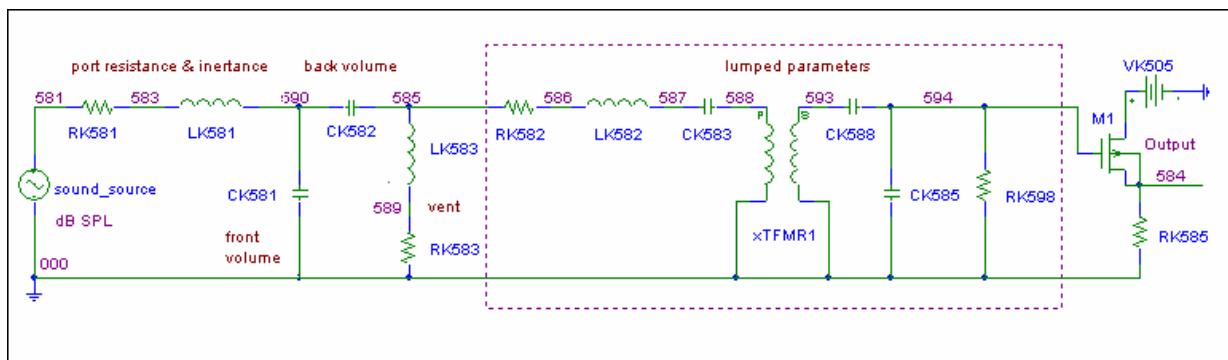



FIG. 2a: Schematic of a Knowles microphone analog.

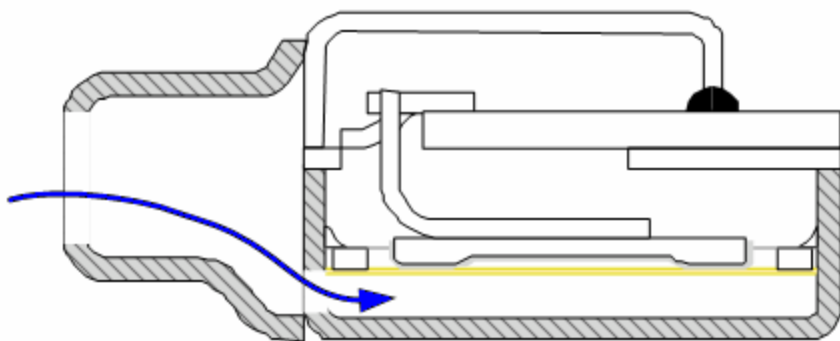

**FIG. 2b:** Cross-section of EM microphone showing acoustical elements that correspond to components in the analog (i.e., components in Figure 2a).


### Receiver Analog

The receiver analog is represented schematically in Fig. 3. The motor in the receiver (i.e., coil, armature, etc.) converts electrical and magnetic energy into mechanical energy (force, velocity) then the diaphragm converts mechanical energy (force, velocity) into acoustic energy (pressure, volume velocity).

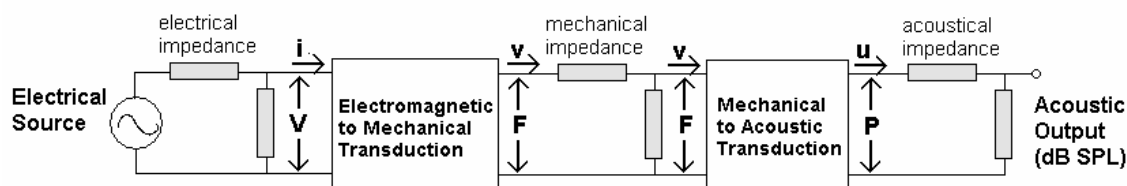


**FIG. 3:** Electrical  $\Leftrightarrow$  magnetic  $\Leftrightarrow$  mechanical  $\Leftrightarrow$  acoustical transduction

The circuit topology for a receiver analog is shown in Fig. 4a. On the acoustic side (i.e., to the right of the gyrator), some of the components are the same as the microphone (i.e., front volume, back volume, etc.). Like the microphone analog, receiver components have been combined to reduce the size of the circuit and are labeled “lumped parameters”. Since the circuit components are combined there is no longer a one to one correspondence to the parts in the receiver. Most module files and subcircuit definitions use the same circuit topology, component names, and node numbers shown in Fig. 4.

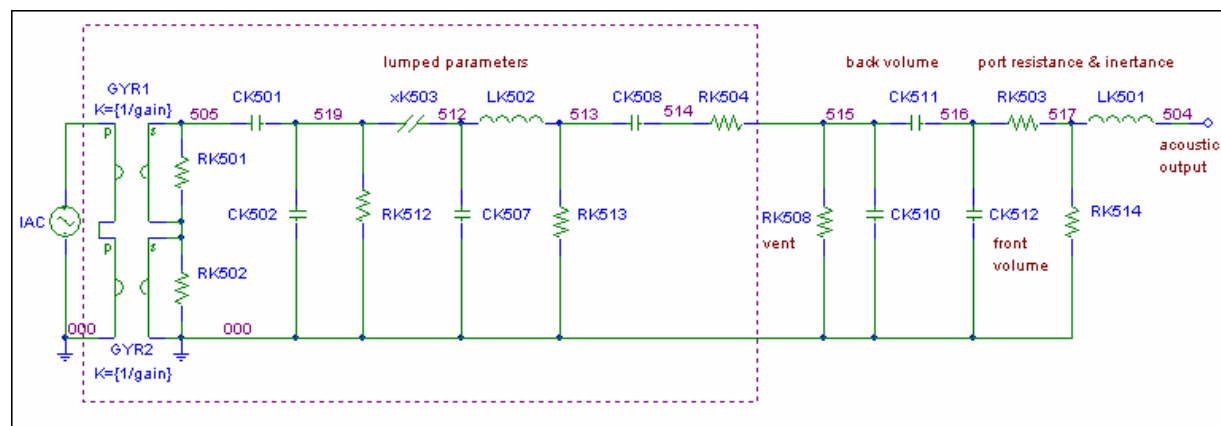

**FIG. 4a:** Schematic of a Knowles Receiver analog.

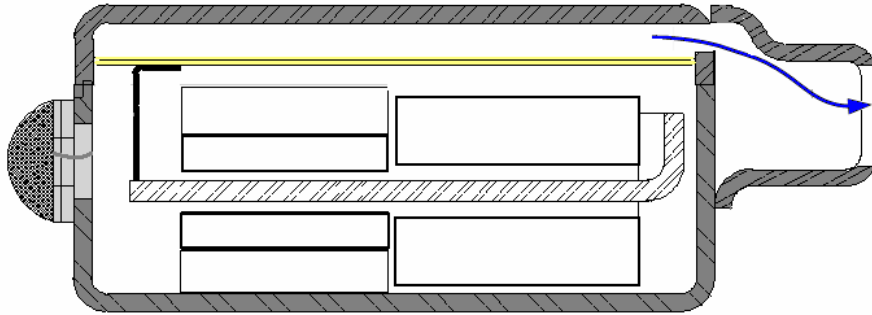

**FIG. 4b:** Cross-section of ED receiver showing elements that correspond to components in the analog (i.e., components in Figure 4a).

**Analog only approximate the behavior of the devices they are to simulate.** These circuits are linear. They apply only at power levels within the linear capabilities of the devices they simulate. They cannot simulate any non-linearity or power limitation in the device. The performance of these modules outside of the range 100 Hz to 10 kHz may be unpredictable.

### III Netlist Modules and Libraries

Electrical Analogs for Knowles Electronics Transducers are designed to be used with a PSpice circuit analysis program. The complete set contains over 300 transducer analogs.

- Modules for building netlists<sup>1</sup> (\*.TXT)
- Library files for Orcad Schematics<sup>2</sup> (\*.SLB, \*.LIB)
- Schematics files for Orcad Schematics (\*.SCH)
- PDF copy of the circuit schematic (\*.PDF)
- Library files for Orcad Capture (\*.OLB, \*.LIB)

The .LIB library files are text files containing subcircuit definitions of the transducers (e.g., ke.FC.LIB for FC receiver analogs). The subcircuits use the standard PSpice format. Even if you are not using the Orcad circuit simulator, you can use the subcircuits to create parts for your circuit program.


#### Node Numbering, Device Specifications, & Modules

Appendix F contains detailed information on node numbers and device specifications for the Knowles analogs. This section contains a brief overview.

- All device and node numbers are in the range 400 to 699.
- To distinguish parts of these analogs from others in your application, all device specifications have the letter 'K' after the reserved device specifying letter. That is, all capacitor devices in the analog have a designation such as CK5xx.
- The programs are grouped by functional modules or subcircuits. Each module has a generic name and a serial identification. The block diagrams in Fig. 5 show the layout of nodes for attachment to the program modules that are provided.

<sup>1</sup> Module files are text files that contain the .SUBCKT and .MODEL definitions of the transducers and the components. The same SUBCKT and MODEL definitions are also found in the \*.LIB files.

<sup>2</sup> Orcad Schematics formerly called Microsim Schematics (identical programs)

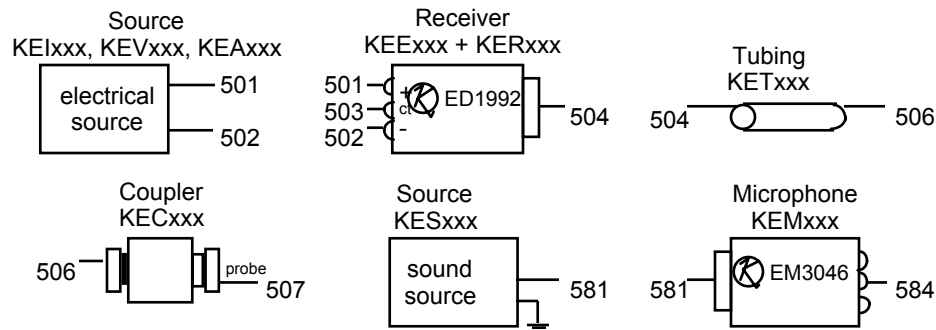


**Fig. 5:** Modules and terminating node numbers for the transducer analogs.

Any PSpice simulation must contain the appropriate combination of modules. The use of modules such as KETxxx (tubing), KECxxx (coupler) and/or KEFxxx (end of file statement) are optional, depending on the nature of the simulation. For example, to generate a receiver's response curve found on the Knowles product specifications Sheet 2.1, you need a current source, the electrical and mechanical components of the receiver, tubing, and a coupler cavity. The modules that are needed to simulate an ED-21913 in its Sheet 2.1 configuration are shown in Fig. 6a. The same simulation is shown using parts from the library files for Orcad Schematics Capture (Fig. 6b).

#### 2a. Netlist Modules



#### 2b. Schematics Parts

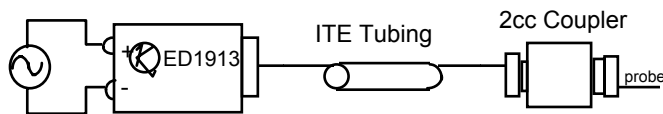

**Fig. 6:** Netlist modules and Schematics Capture parts to simulate the Knowles Electronics 2.1 sheet specification for ED-21913 receiver.

#### Receiver Subcircuits

A receiver requires two modules: KEExxx and KERxxx. The two-part model allows many combinations of coils and damping within one series of receivers. The library files (\*.LIB) define all of the modules as subcircuits. The \*.SLB and \*.OLB library files contain the part symbol, pin attributes, and links the symbol to the subcircuits. Appendix A. has a list of all available transducer models and their associated subcircuit modules (i.e., module name + serialized number)

Receiver subcircuit in the keED.LIB library:

```
.SUBCKT ED21913 501 502 504
xKEE 501 502 503 505 KEEED1
xKER 505 504 KERED1
.ENDS
```

Subcircuit name =	ED21913
Input nodes (+) and (-) =	501 and 504
Output node (pressure & volume velocity) =	504
Coil subcircuit =	keeED1
Receiver subcircuit =	kerED1

**When the input is in terms of volts and amperes the output energy is in terms of watt-seconds. To convert a node voltage to dB SPL you must add 144 dB.** The usual query would be DB(V(507))+144 (or DBV(507)+144) for the SPL in a coupler. (70 dB of this factor is to change from a watt-second to an erg reference frame and 74 dB to change from dynes/cm<sup>2</sup> to 0.0002 dynes/cm<sup>2</sup> which is the 0 dB SPL reference level.). The 70dB factor is a consequence of using cgs units for acoustical and mechanical analogs (i.e., centimeter-gram-second unit system).

#### Microphone Subcircuits

The microphone modules have the designation KEMxxx. The device designations follow the convention used for receivers. All Knowles microphones are active devices. No attempt has been made to simulate the D.C. voltage levels. There is no substantial bidirectional interaction between the acoustical and electrical portions of the analog. Unlike the receiver subcircuit, the microphone subcircuit

Microphone subcircuit in the keEM.LIB library:

```
*KEMEM10, EM-23346
.SUBCKT EM3346      581 584
RK581              581 583 2.55E+3
RK582              585 586 0.95E+3
(Deleted components in this example)
M1                 596 594 584 584 MOS_2
VK505              596 0 1.5
.ENDS
```

Subcircuit name = EM3346  
Input nodes (pressure & volume velocity) = 581  
Output node (+) = 584

The applied voltage is numerically equal to the applied sound pressure in dynes/cm<sup>2</sup> (i.e., 1 volt is equivalent to 74dB SPL). The electrical output signal is volts and /or amperes. **70 dB must be subtracted from the output voltage** or scale the input voltage by -70dB (i.e., scale sound source by 1/3162). The 70 dB of this factor is to change from a watt-second to an erg reference frame. The sound pressure is referenced to node 0 (i.e., ground). The electrical output signal is also referenced to node 0.

#### Circuit Components, Tubes and Coupler Cavities

The analogs are built from standard circuit components (i.e., R, L and C) and custom circuit components (Table 1.). In the analog modules, these non-standard components are defined in subcircuit statements. The same components can also be found in the KNOWLES.SLB and KNOWLES.LIB libraries.

Subcircuit / Component Name	
Ideal Transformer	TFMR
Gyrator (k= 1/gain)	GYR
Semi-capacitance ( $\propto 1/\sqrt{j \cdot \omega}$ )	CMAG
Semi-inductance ( $\propto \sqrt{j \cdot \omega}$ )	LMAG

**TABLE 1.:** Non-standard circuit components

The available tube models, special tubing, and coupler cavities are listed in Table 2. Analogs Release 8 or newer include new tube model. The new tube model does not have the length limitation of the older model. In addition, length and radius are changeable parameters.



Tube Segments (variable length and radius)	Tube_cgs, Tube_SI (new)
Special Tubing (per Knowles specifications)	ITE and BTE
Coupler Cavities	IEC 711, Zwislocki ear simulator, and 2cm <sup>3</sup>

**TABLE 2.:** Tubing and couplers


It may be necessary to load the obsolete tube models for older schematics. The tube parts and subcircuits were deleted from the KNOWLES.SLB and the KNOWLES.LIB files and moved to separate library files appropriately named “Old tube models.slb” and “Old tube models.lib”.

#### IV. Schematics and Capture Libraries

The electrical analogs of Knowles Electronics transducers can be added to the Parts Browser of Orcad Schematics and Capture. To place a transducer on your schematic, simply type the Knowles part number into the Parts Browser without a dash (e.g., ED21913). The analog libraries consist of subcircuit definitions which are identical to the netlist modules. The KNOWLES library contains parts that simulate standard Knowles ITE and BTE tubing, 2cm<sup>3</sup> coupler cavity, IEC 711 or Zwislocki ear simulators, and more. The receiver and microphone libraries are organized according to the series name. For example, the ED-21913 analog is in the “keED” library. All analogs require both symbol library (e.g., \*.SLB for Schematics or \*.OLB for Capture) and model library (e.g., \*.LIB) to run. Follow the directions in Appendix C to configure Schematics and Capture to use these libraries.

##### Receivers

The receiver analogs libraries are organized according to series (e.g., keED.lib, keFC.lib, etc.). When the input is in terms of volts or amperes the output energy is in terms of watt-seconds. **To convert the output voltage to dB SPL, add 144 dB.** 70dB is added to change from watt-second to erg and 74dB is added to change from dyne/cm<sup>2</sup> to 0.0002 dynes/cm<sup>2</sup> which is the 0 dB SPL reference level. The setup that is shown in Fig. 7 will generate the response curve for the ED-21913 receiver found in the Knowles product specification Sheet 2.1. The voltage on the ‘probe’ pin of the 2cc Coupler is equal to the sound pressure at the reference microphone in the coupler. Place a VdB marker (i.e., voltage probe) on this pin. To convert the output voltage of this model to dB SPL, double click on the trace in Probe and type the following: VDB(2cc\_Coupler:pin2)+144.

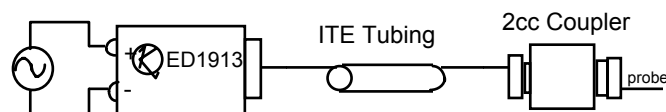

**FIG. 7.:** Example schematic

##### Microphones

The microphone analogs libraries are also organized according to series (e.g., keEM.lib, keFG.lib, etc.). The applied voltage is equal to the applied sound pressure in dynes/cm<sup>2</sup> (i.e., 1 volt is equivalent to 74dB SPL). The electrical output signal is volts or amperes. **70 dB must be subtracted from the output voltage** or scale the input voltage by -70dB (i.e., scale sound source by 1/3162). The sound pressure is referenced to node 0 (i.e., ground). The electrical output signal is also referenced to node 0. See Appendix D for more information on noise modeling.

#### V. ACOUSTIC TRANSMISSION TUBES

Tubes are one of the most popularly used acoustic elements in acoustic designs. The acoustic properties of tubes were studied as early as the era of Helmholtz [1], Kirchhoff [2], and Rayleigh [3]. The first approximation of the full Kirchhoff solution was given by Kirchhoff [2] himself for “wide” tubes and by Rayleigh [3] for “narrow” tubes. However, those solutions are Bessel functions with complex argument, which are difficult to deal with in old days. In fact, even today they are not easy to implement in programs such as PSpice. Effort has been made in simplifying the solutions [4, 5, 6]. The original tube models by Knowles were based on the work by Zuercher [7] who obtained quite simple algebraic expressions that can accurately approximate (with discrepancies being less than 3%) the value of the acoustic impedance of small tubes (radii less than 1/16 acoustic wavelength) including isothermal and

viscous effects. However, the older PSpice model has limitations: 0.2cm length limit per segment and fixed diameter. Recently, PSpice has become more powerful and it provides the users the Analog Behavior Modeling (ABM) feature. Applying this feature, we have built a tube acoustic model that is more meaningful and more accurate using piecewise functions.

The tube models are available as library parts for Schematics and Capture. Build any tubing by simply entering in the length and diameter for each segment. The PARAMS: LEN (length) and RAD (radius) are expressed in centimeters for Tube\_cgs and meters for Tube\_SI.

## VI. HELPFUL HINTS AND TROUBLESHOOTING

### Converting Analogs to Subcircuits for Other Programs

The analogs can be integrated into an electronic circuit (netlist), *filename.CIR*, using any text editor. This circuit file can be read directly by PSpice without use of a schematics program. To convert an analog into a part for a different schematics program, you need to find the subcircuit and to create a symbol or package. The transducer subcircuits can be found in the \*.LIB library files which can be opened with a text editor. For example, the analog for the EM-3046 microphone in keEM.LIB is shown below:

```
*KEMEM1, EM-3046
*EM-PA (standard response, 12B port, WS)
.SUBCKT KEMEM1      581 584

RK581      581 583  1.85E+3
RK582      585 586  1.00E+3
RK583      589   0  33.0E+3
RK585       0 584  22E+3
RK586       0 594  7.0E+9
RK587      595 594  1.0E+12
RK591      595 584  1.0E+6
RK593      594 596  1E4
RK592      594 596  1E4
CK581       0 590  1.20E-9
CK582      585 590  8.80E-9
CK583      587 588  12.0E-9
CK585       0 594  1.42E-12
CK587      595 594  1.60E-12
CK586      584 594  3.20E-12
CK588      593 594  -0.77E-12
LK581      583 590  8.50E-2
LK582      586 587  2.65E-2
LK583      585 589  1.00E-2
xTFMR1      593   0 588   0 TFMR PARAMS: PRI=261.55, SEC=1
GK581      595 584 596 584 .325E-3
VK581      595   0  AC .000E+1
.ENDS

.SUBCKT TFMR      1   2   3   4   PARAMS:PRI=1, SEC=1
R1  1   2   1E+12
R3  3   4   1E+12
V1  1   5
G1  4   3   VALUE = {I(V1)*PRI/SEC}
E1  5   2   VALUE = {V(3,4)*PRI/SEC}
.ENDS
```

The first step is to create a new symbol / package for the microphone. The symbol can be a box with two pins. The pins must be correctly mapped to the input (581) and output (584) nodes of the microphone subcircuit (i.e., Pin 1 = 581, Pin 2 = 584). The symbol or package must also reference the subcircuit. Otherwise, you will see the part on your schematic but you will not be able to run a simulation. Remember that you will also need to have subcircuit statements for any nonstandard components such as CMAG and TFMR. You do not need to create symbols but the subcircuit statements should be in the same library as your transducer. It may be helpful to refer to your software manuals for more information on netlists and subcircuit definitions.

### **Converting CGS ⇔ SI Units**

Historically, all Knowles' analogs use CGS units. This practice dates back to the time when analogs were built using real components. The CGS unit system has been maintained for new analogs as well. The advantage of CGS units is the component values are more typical of real-life devices. High resistor values in SI units can lead to simulation errors in some programs (e.g., bias point or convergence errors). The disadvantage of CGS is the correction factors for receivers (+70dB) and microphones (-70dB). In SI units, you need only add 94dB to the output of a receiver to convert dB Pa to dB SPL. The output of the microphone requires no change.

A CGS acoustical ohm has units of  $Z_{CGS} = \text{gm}/(\text{cm}^4 * \text{sec})$ . In order to convert the components to SI units  $Z_{SI} = \text{kg}/(\text{m}^4 * \text{sec})$ , scale the acoustical impedances:  $Z_{SI} = Z_{CGS} * 10^5$ .

#### ***Pressure***

##### **CGS Units**

0.1 Pa = 1.0 volt

##### **SI Units**

0.1 Pa = 0.1 volt

#### ***Receivers***

- Acoustical impedance:  $Z_{SI} = Z_{CGS} * 10^5$  ( $R * 10^5$ ,  $L * 10^5$ , &  $C / 10^5$ )
- Correct the gain of the voltage controlled current sources:
  - GK501 and 503 =>  $\text{gain}_{SI} = \text{gain}_{CGS} / [\text{sqrt}(10^5)]$
  - GK502 and 504 =>  $\text{gain}_{SI} = \text{gain}_{CGS} / [\text{sqrt}(10^5)]$
- Increase values of resistors RK509, RK510, RK511 from 0.1E+9 to 0.1E+12. Lower values cause error in input impedance (i.e., raises DCR). Higher values may cause convergence errors during simulations.
- Add 94dB to convert dB V at output to dB SPL (i.e., 1 V = 1 Pa).

#### ***Microphones***

- Acoustical impedance:  $Z_{SI} = Z_{CGS} * 10^5$  ( $R * 10^5$ ,  $L * 10^5$ , &  $C / 10^5$ )
- Correct turns ratio of transformer:  $N(\text{sec}) / \text{sqrt}(10^5)$
- 74 dB sound source is represented by a 0.1 V voltage source (i.e., 0.1 Pa = 0.1 V).

### **Micro-Cap Circuit Simulator – Known Conflicts**

If you use Micro-Cap, there are some known conflicts:

- The negative terminal in the receiver analogs (i.e., node 502) must be grounded due to differences in the voltage controlled current source model (i.e., grounding not required in Orcad Schematics or Capture).
- The comma was removed from the transformer subcircuit (i.e., TFMR) "PARAM" statement to fix a MicroCAP error message. The comma between parameters is optional in PSpice and does not affect Orcad.  
xTFMR1 593 0 588 0 TFMR PARAMS: PRI=261.55, SEC=1  
changed to:  
xTFMR1 593 0 588 0 TFMR PARAMS: PRI=261.55 SEC=1
- Equal sign was added to the tube subcircuits in the KNOWLES.LIB file. The missing "=" caused an error in MicroCap. Orcad Schematics will run with or without the "=" sign:  
GR1 1 5 FREQ {V(1,5)/LREF}=
- The CMAG subcircuit causes an error "no DC path to ground" in Micro-Cap. The CMAG subcircuit has NOT been changed. Replace the CMAG circuit with this revised version:  
.SUBCKT CMAG 1 2 PARAMS:CMAG = 1  
R1 1 2 1E+9

```

EB 3 0 VALUE={.707*V(1,2)*CMAG*6282}
G1 1 2 FREQ {V(3,0)} =
+ (20,-17,45)
+ (20000,13,45)
.ENDS

```

### Transient Analysis and CMAG Component


CMAG is a special “semi-capacitance” used in the magnetic modeling of receivers. It represents the  $1/\sqrt{f}$  eddy current loss in magnetic materials. The CMAG subcircuit is defined by a look-up table that can cause errors when a transient analysis is run. The CMAG subcircuit can be replaced by the ladder network, which is shown in Figure 8 (cgs units).

EK = voltage controlled voltage source

FK = current controlled current source

Set gain for EK and FK equal to:  $\text{Gain} = 1/\sqrt{6283.2 \cdot \text{CMAG}} = 0.012616/\sqrt{\text{CMAG}}$

Example: CI analog:  $\text{CMAG} = 0.107\text{E-}6$ ,  $\text{Gain} = 38.6$

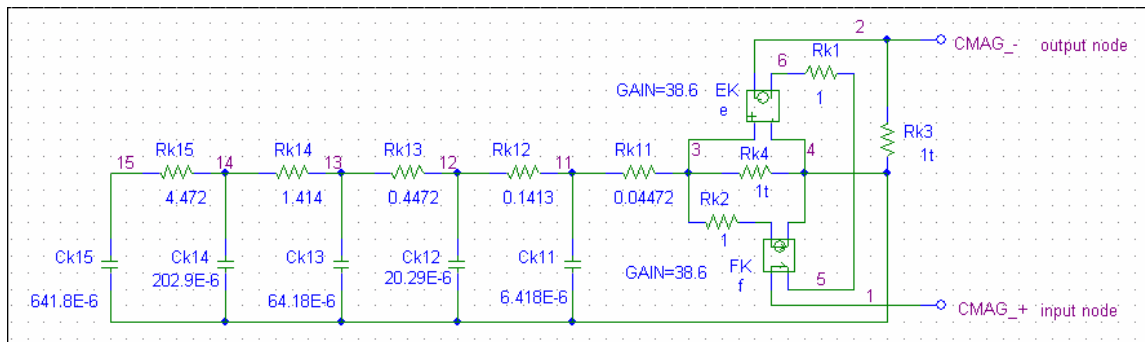

**FIG.8:** Ladder network that can replace CMAG component.

### References from Tube Model section:

- [1] H. L. F. Helmholtz, “On the Influence of Friction in the Air on Sound Motion,” Verh. Natur. Histor. Medizin. Ver Heidelberg III, 16 (1863)
- [2] G. R. Kirchhoff, “On the Influence of Thermal Conduction in a Gas on the Motion of Sound,” Poffendorfer Ann. 134, 177-193 (1868)
- [3] Lord Rayleigh, Theory of Sound Volume II (The Macmillan Company, London, Second Edition)
- [4] A. H. Benade, “On the Propagation of Sound Waves in a Cylindrical Conduit,” J. Acoust. Soc. Am. 44, 616-623 (1968)
- [5] H. Tijdeman, “On the propagation of sound waves in cylindrical tubes,” J. Sound and Vib. 39(1), 1-33 (1974)
- [6] Douglas H. Keefe, “Acoustical wave propagation in cylindrical ducts: Transmission line parameter approximations for isothermal and nonisothermal boundary conditions,” J. Acoust. Soc. Am. 75, 58-62 (1984)
- [7] Joseph C. Zuercher, Elmer V. Carlson, and Mead C. Killon, “Small acoustic tubes: New Approximations including isothermal and viscous effects,” J. Acoust. Soc. Am. 83(4), 1653-1660 (1984)

### Acknowledgments & Comments:

E. V. Carlson began this project and released Revision #1 of the Knowles Electronics, Inc. Analogs in 1991. The analogs have continued to evolve and to be revised. The current collection contains over 300 analogs. If you have any suggestions, questions, or problems, please contact me.

J. L. LoPresti (janice.lopresti@knowles.com)

# Appendix A

## Catalog of Available Transducer Analogs

All transducer analogs are listed in this appendix grouped by transducer type (receiver or microphone) and series designation (ED, EM, etc.). All part numbers have been updated to reflect the new Knowles 5-digit numbering system.

### Changes in Release 9.0

- Newer product families added to collection: WBHC, WBFK, TWFK, TEC, DTEC
- Subcircuit names reflects current Knowles part number system
- Coil model for receivers corrected to ensure proper polarity per Sheet 1.1 specifications
- Old tube models deleted from “KNOWLES” library and moved to separate “OLD TUBE MODELS” library

### RECEIVERS

MODEL #	KEExxx	KERxxx	Nominal Drive	Tubing	# Pads
BK-21600	keeBK1	kerBK1	1.00 mA	BTE (HA-2 coupler)	2
BK-21604	keeBK16	kerBK1	0.33 mA	BTE (HA-2 coupler)	2
BK-21606	keeBK10	kerBK1	0.71 mA	BTE (HA-2 coupler)	2
BK-21610	keeBK2	kerBK1	0.45V, 50 Ohm	BTE (HA-2 coupler)	2
BK-21612	keeBK12	kerBK1	0.55 mA	BTE (HA-2 coupler)	2
BK-21613	keeBK9	kerBK1	0.78 mA	BTE (HA-2 coupler)	3
BK-21615	keeBK9	kerBK1	0.78 mA	BTE (HA-2 coupler)	3
BK-21618	keeBK10	kerBK1	0.71 mA	BTE (HA-2 coupler)	2
BK-21669	keeBK17	kerBK1	3.61 mA	BTE (HA-2 coupler)	2
BK-21706	keeBK6	kerBK1	1.20 mA	BTE (HA-2 coupler)	3
BK-21888	keeBK7	kerBK2	1.73V, 890 Ohm	BTE	3
BK-21968	keeBK1	kerBK1	1.00 mA	BTE (HA-2 coupler)	3
BK-28507	keeBK18	kerBK2	0.35V, 30 Ohm	BTE	2
CI-22746	keeCI3	kerCI1	2.40 mA	BTE	3
CI-22748	keeCI2	kerCI1	2.00 mA	BTE	3
CI-22762	keeCI3	kerCI1	2.40 mA	BTE	3
CI-22764	keeCI2	kerCI1	2.00 mA	BTE	3
CI-22955	keeCI4	kerCI1	3.75 mA	BTE	3
CI-22960	keeCI1	kerCI1	1.60 mA	BTE	3
CI-28203	keeCI7	kerCI1	2.00 mA	BTE	3
CI-28204	keeCI1	kerCI1	1.60 mA	BTE	3
CI-28220	keeCI4	kerCI1	3.75 mA	BTE	3
CI-28226	keeCI7	kerCI1	2.00 mA	BTE	3
CI-28267	keeCI7	kerCI1	2.00 mA	BTE	3
CI-28268	keeCI3	kerCI1	2.40 mA	BTE	3
CI-28329	keeCI3	kerCI1	2.40 mA	BTE	3
CI-28352	keeCI4	kerCI1	3.75 mA	BTE	3
CI-28409	keeCI1	kerCI1	1.60 mA	BTE	3
CI-28417	keeCI4	kerCI1	3.75 mA	BTE	2
CI-28434	keeCI6	kerCI1	3.18 mA	BTE	2
CI-28487	keeCI6	kerCI1	3.18 mA	BTE	3
dTEC-30008	dttec30008		.154 V	BTE	4
EC-23095	keeEC2	kerEC1	0.54 mA	10mm x 1mm ID	2
EC-23096	keeEC1	kerEC1	0.77 mA	10mm x 1mm ID	2

EC-23097	keeEC3	kerEC1	1.09 mA	10mm x 1mm ID	2
EC-23098	keeEC1	kerEC1	0.77 mA	10mm x 1mm ID	3
EC-23104	keeEC2	kerEC1	0.54 mA	10mm x 1mm ID	3
ED-21739	keeED1	kerED3	0.50 mA	10mm x 1mm ID	2
ED-21744	keeED5	kerED3	0.35 mA	10mm x 1mm ID	3
ED-21912	keeED2	kerED1	0.70 mA	10mm x 1mm ID	2
ED-21913	keeED1	kerED1	0.50 mA	10mm x 1mm ID	2
ED-21914	keeED5	kerED1	0.35 mA	10mm x 1mm ID	2
ED-21915	keeED7	kerED1	0.25 mA	10mm x 1mm ID	2
ED-21925	keeED3	kerED1	0.88 mA	10mm x 1mm ID	2
ED-21932	keeED2	kerED1	0.70 mA	10mm x 1mm ID	3
ED-21950	keeED3	kerED2	0.88 mA	10mm x 1mm ID	3
ED-21975	keeED1	kerED1	0.50 mA	10mm x 1mm ID	2
ED-21983	keeED2	kerED2	0.70 mA	10mm x 1mm ID	2
ED-21985	keeED7	kerED2	0.25 mA	10mm x 1mm ID	2
ED-21987	keeED7	kerED3	0.25 mA	10mm x 1mm ID	2
ED-21992	keeED2	kerED3	0.70 mA	10mm x 1mm ID	3
ED-23004	keeED1	kerED3	0.50 mA	10mm x 1mm ID	3
ED-23009	keeED7	kerED3	0.25 mA	10mm x 1mm ID	3
ED-23012	keeED2	kerED3	0.70 mA	10mm x 1mm ID	2
ED-23087	keeED1	kerED4	0.50 mA	10mm x 1mm ID	3
ED-23088	keeED3	kerED3	0.88 mA	10mm x 1mm ID	3
ED-23093	keeED2	kerED4	0.70 mA	10mm x 1mm ID	3
ED-23099	keeED5	kerED4	0.35 mA	10mm x 1mm ID	2
ED-23100	keeED7	kerED4	0.25 mA	10mm x 1mm ID	2
ED-23145	keeED1	kerED1	0.50 mA	10mm x 1mm ID	2
ED-23146	keeED14	kerED1	1.00 mA	10mm x 1mm ID	2
ED-23147	keeED10	kerED1	2.00 mA	10mm x 1mm ID	2
ED-23162	keeED10	kerED3	2.00 mA	10mm x 1mm ID	2
ED-27045	keeED2	kerED1	0.70 mA	10mm x 1mm ID	3
ED-27055	keeED7	kerED1	0.25 mA	10mm x 1mm ID	2
ED-27288	keeED11	kerED3	1.98 mA	10mm x 1mm ID	2
ED-27304	keeED12	kerED4	1.00 mA	10mm x 1mm ID	2
ED-27305	keeED11	kerED4	1.98 mA	10mm x 1mm ID	2
ED-27398	keeED2	kerED2	0.43 V	10mm x 1mm ID	2
ED-27488	keeED2	kerED3	0.70 mA	10mm x 1mm ID	2
ED-28331	keeED5	kerED4	0.35 mA	10mm x 1mm ID	3
ED-29689	keeED9	kerED1	6.30 mA	10mm x 1mm ID	3
EF-21763	keeEF1	kerEF1	0.85 mA	BTE	2
EF-21933	keeEF1	kerEF1	0.85 mA	BTE	3
EF-21935	keeEF3	kerEF1	1.56 mA	BTE	3
EF-21937	keeEF2	kerEF1	1.13 mA	BTE	3
EF-21942	keeEF2	kerEF1	1.13 mA	BTE	2
EF-21943	keeEF2	kerEF1	1.13 mA	BTE	3
EF-21958	keeEF1	kerEF1	0.85 mA	BTE	3
EF-23025	keeEF3	kerEF1	1.56 mA	BTE	3
EF-23094	keeEF2	kerEF1	1.13 mA	BTE	3
EF-23168	keeEF6	kerEF4	0.33 V	BTE	2
EF-26161	keeEF5	kerEF1	1.27 mA	BTE	2
EF-26348	keeEF8	kerEF6	0.14 V	BTE	2
EF-26356	keeEF8	kerEF6	0.14 V	BTE	2
EF-26363	keeEF9	kerEF1	2.49 mA	BTE	2
EF-26665	keeEF12	kerEF1	1.15mA	BTE	2
EF-27428	keeEF2	kerEF1	1.13 mA	BTE	3
EF-27534	keeEF7	kerEF1	2.82 mA	BTE	2

EF-27715	keeEF3	kerEF1	1.56 mA	BTE	3
EF-28321	keeEF1	kerEF1	0.85 mA	BTE	3
EF-29615	keeEF3	kerEF1	1.56 mA	BTE	3
EF-29734	keeEF3	kerEF1	1.56 mA	BTE	3
EF-29802	keeEF10	kerEF1	0.5 mA	BTE	3
EH-23030	keeEH1	kerEH1	0.71 mA	10mm x 1mm ID	2
EH-23043	keeEH1	kerEH2	0.71 mA	10mm x 1mm ID	2
EH-23044	keeEH1	kerEH1	0.71 mA	10mm x 1mm ID	2
EH-23048	keeEH3	kerEH1	0.61 mA	10mm x 1mm ID	2
EH-23050	keeEH2	kerEH1	1.03 mA	10mm x 1mm ID	2
EH-23052	keeEH4	kerEH1	0.51 mA	10mm x 1mm ID	2
EH-23053	keeEH4	kerEH2	0.51 mA	10mm x 1mm ID	2
EH-23054	keeEH1	kerEH1	0.71 mA	10mm x 1mm ID	2
EH-23061	keeEH2	kerEH2	1.03 mA	10mm x 1mm ID	3
EH-23063	keeEH1	kerEH2	0.71 mA	10mm x 1mm ID	3
EH-23066	keeEH5	kerEH1	0.43 mA	10mm x 1mm ID	2
EH-23067	keeEH5	kerEH2	0.43 mA	10mm x 1mm ID	2
EH-27157	keeEH1	kerEH2	0.71 mA	10mm x 1mm ID	2
EH-27232	keeEH6	kerEH6	1.63 mA	10mm x 1mm ID	2
EH-27250	keeEH5	kerEH1	0.43 mA	10mm x 1mm ID	2
EH-29833	keeEH2	kerEH2	1.03 mA	10mm x 1mm ID	2
EP-24073	keeEP1	kerEP1	0.032 V	10mm x 1mm ID	3
EP-24074	keeEP4	kerEP1	0.032 V	10mm x 1mm ID	3
EP-24075	keeEP5	kerEP1	0.032 V	10mm x 1mm ID	3
EP-24106	keeEP1	kerEP3	0.032 V	10mm x 1mm ID	3
EP-24107	keeEP4	kerEP3	0.032 V	10mm x 1mm ID	3
EP-24108	keeEP5	kerEP3	0.032 V	10mm x 1mm ID	3
EP-24123	keeEP1	kerEP2	0.032 V	10mm x 1mm ID	3
EP-24124	keeEP4	kerEP2	0.032 V	10mm x 1mm ID	3
EP-24125	keeEP5	kerEP2	0.032 V	10mm x 1mm ID	3
EP-24135	keeEP1	kerEP6	0.032 V	10mm x 1mm ID	3
EP-24136	keeEP4	kerEP4	0.032 V	10mm x 1mm ID	3
EP-24137	keeEP5	kerEP4	0.032 V	10mm x 1mm ID	3
EP-27103	keeEP2	kerEP1	0.032 V	10mm x 1mm ID	3
EP-27104	keeEP3	kerEP1	0.032 V	10mm x 1mm ID	3
EP-27107	keeEP2	kerEP3	0.032 V	10mm x 1mm ID	3
EP-27108	keeEP3	kerEP3	0.032 V	10mm x 1mm ID	3
EP-27109	keeEP2	kerEP2	0.032 V	10mm x 1mm ID	3
EP-27110	keeEP3	kerEP2	0.032 V	10mm x 1mm ID	3
EP-27202	keeEP2	kerEP6	0.032 V	10mm x 1mm ID	3
EP-27284	keeEP3	kerEP4	0.032 V	10mm x 1mm ID	3
ES-23126	keeES1	kerES1	0.025 V	10mm x 1mm ID	3
ES-23127	keeES2	kerES1	0.025 V	10mm x 1mm ID	3
ES-23139	keeES1	kerES2	0.025 V	10mm x 1mm ID	3
ES-23140	keeES2	kerES2	0.025 V	10mm x 1mm ID	3
ES-23153	keeES1	kerES4	0.025 V	10mm x 1mm ID	3
ES-23154	keeES2	kerES4	0.025 V	10mm x 1mm ID	3
ES-23166	keeES1	kerES1	0.025 V	10mm x 1mm ID	3
ES-23167	keeES2	kerES1	0.025 V	10mm x 1mm ID	3
ES-23171	keeES1	kerES3	0.025 V	10mm x 1mm ID	3
ES-23172	keeES2	kerES3	0.025 V	10mm x 1mm ID	3
ES-23174	keeES1	kerES2	0.025 V	10mm x 1mm ID	3
ES-23175	keeES2	kerES2	0.025 V	10mm x 1mm ID	3

FC-23265	keeEH1	kerFC2	0.71 mA	10mm x 1mm ID	2
FC-23300	keeEH1	kerFC1	0.71 mA	10mm x 1mm ID	2
FC-23306	keeEH5	kerFC2	0.43 mA	10mm x 1mm ID	2
FC-26170	keeFC2	kerFC5	0.81 mA	10mm x 1mm ID	2
FC-26171	keeFC1	kerFC5	1.63 mA	10mm x 1mm ID	2
FC-26184	keeFC3	kerFC5	1.02mA	10mm x 1mm ID	2
FC-26314	keeEH6	kerFC6	1.63 mA	10mm x 1mm ID	2
FC-26654	keeFC4	kerFC5	2.41 mA	10mm x 1mm ID	2
FD-23266	keeFD1	kerFD1	0.025 V	10mm x 1mm ID	3
FD-23283	keeFD2	kerFD1	0.025 V	10mm x 1mm ID	3
FD-23284	keeFD1	kerFD2	0.025 V	10mm x 1mm ID	3
FD-23285	keeFD2	kerFD2	0.025 V	10mm x 1mm ID	3
FH-23371	keeFH2	kerFH1	1.59 mA	10mm x 1mm ID	2
FH-23373	keeFH3	kerFH1	1.14 mA	10mm x 1mm ID	2
FH-23375	keeFH1	kerFH1	0.80 mA	10mm x 1mm ID	2
FH-23377	keeFH4	kerFH1	0.56 mA	10mm x 1mm ID	2
FK-23451	keeFK1	kerFK1	0.50 mA	10mm x 1mm ID	2
FK-23466	keeFK1	kerFK1	0.50 mA	10mm x 1mm ID	2
FK-23989	keeFK6	kerFK1vented	0.085 V	10mm x 1mm ID	2
FK-30018	keeFK4	kerFK1vented	0.174 V	10mm x 1mm ID	2
HC-23761	keeHC1	kerHC1	0.060 V	10mm x 1mm ID	2
HC-23762	keeHC2	kerHC1	0.071 V	10mm x 1mm ID	2
HC-23763	keeHC3	kerHC1	0.084 V	10mm x 1mm ID	2
HC-23764	keeHC4	kerHC1	0.100 V	10mm x 1mm ID	2
HC-23765	keeHC5	kerHC1	0.119 V	10mm x 1mm ID	2
HC-23766	keeHC6	kerHC1	0.142 V	10mm x 1mm ID	2
HC-23767	keeHC7	kerHC1	0.169 V	10mm x 1mm ID	2
HC-23724	keeHC8	kerHC1	0.200 V	10mm x 1mm ID	2
HC-23768	keeHC9	kerHC1	0.238 V	10mm x 1mm ID	2
HC-23769	keeHC10	kerHC1	0.283 V	10mm x 1mm ID	2
HC-23770	keeHC11	kerHC1	0.336 V	10mm x 1mm ID	2
HC-23771	keeHC12	kerHC1	0.399 V	10mm x 1mm ID	2
HC-23772	keeHC13	kerHC1	0.475 V	10mm x 1mm ID	2
HC-23773	keeHC14	kerHC1	0.564 V	10mm x 1mm ID	2
HC-23774	keeHC15	kerHC1	0.671 V	10mm x 1mm ID	2
HC-23776	keeHC16	kerHC1	0.797 V	10mm x 1mm ID	2
TEC-30006	keeTEC1	kerTEC1	0.154 V	BTE	2
TEC-30033	keeTEC2	kerTEC1	0.109 V	BTE	2
TWFK-23991	twfk23991	Module file name same as part number.			
TWFK-23992	twfk23992	keTWFK library requires keFK & keWBFK libraries be loaded			
TWFK-30017	twfk30017	LFD analog differs slightly from FK1vented			
WBFK-23990	keewbfkHFD3	kerwbfkHFD1	0.188 V	10mm x 1mm ID	2
WBFK-30019	keewbfkHFD1	kerwbfkHFD1	0.094 V	10mm x 1mm ID	2
WBFK-30058	keewbfkHFD4	kerwbfkHFD1	0.266 V	10mm x 1mm ID	2
WBFK-30095	keewbfkHFD1	kerwbfkHFD1	0.094 V	10mm x 1mm ID	2
WBFK-30000	keeWBFK4	kerWBFK1	0.211 V	10mm x 1mm ID	2
WBFK-30042	keeWBFK4	kerWBFK1	0.211 V	10mm x 1mm ID	2
WBFK-30055	keeWBFK5	kerWBFK1	0.300 V	10mm x 1mm ID	2



WBHC-23902	keeWBHC2	kerWBHC1	0.071 V	10mm x 1mm ID	2
WBHC-23903	keeWBHC3	kerWBHC1	0.084 V	10mm x 1mm ID	2
WBHC-23904	keeWBHC4	kerWBHC1	0.100 V	10mm x 1mm ID	2
WBHC-23905	keeWBHC5	kerWBHC1	0.119 V	10mm x 1mm ID	2
WBHC-23906	keeWBHC6	kerWBHC1	0.142 V	10mm x 1mm ID	2
WBHC-23907	keeWBHC7	kerWBHC1	0.169 V	10mm x 1mm ID	2
WBHC-23908	keeWBHC8	kerWBHC1	0.200 V	10mm x 1mm ID	2
WBHC-23909	keeWBHC9	kerWBHC1	0.238 V	10mm x 1mm ID	2
WBHC-23910	keeWBHC10	kerWBHC1	0.283 V	10mm x 1mm ID	2
WBHC-23911	keeWBHC11	kerWBHC1	0.336 V	10mm x 1mm ID	2
WBHC-23912	keeWBHC12	kerWBHC1	0.399 V	10mm x 1mm ID	2
WBHC-23913	keeWBHC13	kerWBHC1	0.475 V	10mm x 1mm ID	2
WBHC-23914	keeWBHC14	kerWBHC1	0.564 V	10mm x 1mm ID	2
WBHC-26825	keeWBHC10	kerWBHC1	0.283 V	10mm x 1mm ID	2
WBHC-26836	keeWBHC10	kerWBHC1	0.283 V	10mm x 1mm ID	2
WBHC-26892	keeWBHC11	kerWBHC1	0.336 V	10mm x 1mm ID	2

### **FERROFLUID-DAMPED RECEIVERS**

<b>MODEL #</b>	<b>KEExxx</b>	<b>KERxxx</b>	<b>Nominal Drive</b>	<b>Tubing</b>	<b># Pads</b>
<b>FED-21932-i06</b>	keeED2	kerFED6	0.44 V	10mm x 1mm ID	3
FED-21932-i04	keeED2	kerFED4	0.44 V	10mm x 1mm ID	3
FED-21932-i02	keeED2	kerFED2	0.44 V	10mm x 1mm ID	3
<b>FED-23732-i06</b>	keeED2	kerFED6	0.44 V	10mm x 1mm ID	2
FED-23732-i04	keeED2	kerFED4	0.44 V	10mm x 1mm ID	2
FED-23732-i02	keeED2	kerFED2	0.44 V	10mm x 1mm ID	2
<b>FED-23147-i06</b>	keeED10	kerFED6	0.146 V	10mm x 1mm ID	2
FED-23147-i04	keeED10	kerFED4	0.146 V	10mm x 1mm ID	2
FED-23147-i02	keeED10	kerFED2	0.146 V	10mm x 1mm ID	2
<b>FED-29457-i06</b>	keeED2	kerFED6	0.44 V	10mm x 1mm ID	2
FED-29457-i04	keeED2	kerFED4	0.44 V	10mm x 1mm ID	2
FED-29457-i02	keeED2	kerFED2	0.44 V	10mm x 1mm ID	2
<b>FEH-27232-i06</b>	keeEH6	kerFEH6	0.24 V	10mm x 1mm ID	2
FEH-27232-i04	keeEH6	kerFEH4	0.24 V	10mm x 1mm ID	2
FEH-27232-i02	keeEH6	kerFEH2	0.24 V	10mm x 1mm ID	2
<b>FEP-24074-i06</b>	keeEP4	kerFEP6	0.032 V	10mm x 1mm ID	3
FEP-24074-i04	keeEP4	kerFEP4	0.032 V	10mm x 1mm ID	3
FEP-24074-i02	keeEP4	kerFEP2	0.032 V	10mm x 1mm ID	3
<b>FES-23127-i04</b>	keeES2	kerFES4	0.025 V	10mm x 1mm ID	3
FES-23127-i02	keeES2	kerFES2	0.025 V	10mm x 1mm ID	3
<b>FFC-6171-i04</b>	keeFC1	kerFFC34	0.24 V	10mm x 1mm ID	2
FFC-6171-i02	keeFC1	kerFFC32	0.24 V	10mm x 1mm ID	2
<b>FFD-23284-i04</b>	keeFD1	kerFFD4	0.025 V	10mm x 1mm ID	3
FFD-23284-i02	keeFD1	kerFFD2	0.025 V	10mm x 1mm ID	3
<b>FFH-23375-i06</b>	keeFH1	kerFFH6	0.25 V	10mm x 1mm ID	2
FFH-23375-i04	keeFH1	kerFFH4	0.25 V	10mm x 1mm ID	2
FFH-23375-i02	keeFH1	kerFFH2	0.25 V	10mm x 1mm ID	2

## MICROPHONES

All microphone analogs have new circuit topology for noise modeling. However only select models have been verified to have the correct noise spectrum. A “(N)” designation in the third column indicates that an analog will accurately simulate noise. See Appendix D. for more information.

MODEL #	KEMxxx	
EA-21842	kemEA1	
EA-21843	kemEA19	
EA-21845	kemEA20	
EA-21867	kemEA3	
EA-21868	kemEA2	
EA-21939	kemEA8	
EA-21972	kemEA18	
EA-21986	kemEA1	
EA-23003	kemEA9	
EA-23006	kemEA11	
EA-23015	kemEA9	
EK-23024	kemEK1	
EK-23027	kemEK5	
EK-23028	kemEK2	
EK-23029	kemEK3	
EK-23032	kemEK8	
EK-23033	kemEK9	
EK-23092	kemEK7	
EK-23132	kemEK10	
EK-23133	kemEK11	
EL-29924	kemEL.txt	directional
EM-23046	kemEM1	(N)
EM-23047	kemEM2	
EM-23058	kemEM4	
EM-23059	kemEM3	
EM-23346	kemEM10	(N)
EM-23368	kemEM11	(N)
EM-23976	kemEM15	
EM-24346	kemEM12	(N)
EM-24368	kemEM13	(N)
EM-25346	kemEM14	
EM-26739	kemEM16	
EM-26091	kemEM20	directional
FG-23329	kemFG1	(N)
FG-23452	kemFG2	
FG-23453	kemFG3	
FG-23629	kemFG11	
FG-23652	kemFG12	
FG-23653	kemFG14	
FG-26163	kemFG4	
FG-26480	kemFG13	

TM-23546	kemTM1	(N)	
TM-24546	kemTM2	(N)	
TO-24603	keTOTDTP.tx t		
TO-24606	keTOTDTP.tx t		
TD-24607	keTOTDTP.tx t	directional	
Pairs	Omni	Directional	
TP-24612	TO-24606	TD-24607	keTOTDTP.txt

## Appendix B

### List of Special Components

#### Modules / Subcircuits for Tubing, Couplers, and Sources

##### Tubing:

KET001	BTE (ear hook simulator + tubing)	[8mm x 1.0mm ID] + [28mm x 1.5mm ID] + [25mm x 2.0mm ID] + [18mm x 3.0mm ID]
KET002	ITE tubing	[10 mm x 1.0mm ID]
<del>KET003</del>	obsolete	
KET004	no tube	
	BTE (tubing + HA-2 coupler)	[38.1mm x 1.35mm ID] + [18mm x 3.0mm ID]

All KETxxx.TXT modules use NEW tube model subcircuits.

Subcircuits for new tube models available in Knowles.lib (cgs and SI units)

##### Couplers:

KEC001	2cc coupler
KEC002	Zwislocki coupler

Other subcircuits available in Knowles.lib file such as B&K 711 coupler

##### Sources:

KEIxxx	constant current source, where xxx = x.xx mA (035=0.35mA)
KEVxxx	constant voltage source, where xxx = x.xx V (003=0.032V)
KEAxxx	constant power source, where xxx = input resistor (037=368 Ohms, 1mW)
KESxxx	sound source (dB SPL)

##### End of File:

KEF001	.END for circuit with .PROBE
KEF002	.END for circuit

##### Node Numbers:

	<u>range</u>
KEVxxx, KEIxxx, KEAxxx	500-502, 529
KEExxx & KERxxx	501-519
KETxxx	504, 506, 531-559
KECxxx	506, 507, 561-569
KEMxxx	571-599

## Appendix C

### Add Knowles Libraries to Orcad Schematics or Capture Parts Browser

The electrical analogs of Knowles Electronics transducers can be added to the Parts Browser of Orcad Schematics and Orcad Capture. To place a transducer on your schematic, simply type the Knowles part number into the Parts Browser without a dash (e.g., ED1913). The analog libraries consist of subcircuit definitions which are identical to the netlist modules. The KNOWLES.LIB library contains parts that simulate standard ITE and BTE tubing, 2cm<sup>3</sup> coupler cavity, IEC711 and Zwislocki ear simulators, and more. The receiver and microphone libraries are organized according to the series name. For example, the ED1913 analog is in the keED library files (e.g., .SLB, .LIB, and .OLB). All analogs require both symbol libraries (e.g., ED.SLB) and model libraries (e.g., ED.LIB) to run. Follow the directions in the next sections to configure Schematics or Capture to use these libraries.

#### LIBRARY FILES

The Electrical Analogs Release 9 Zip file contains modules and libraries in both Orcad Schematics and Orcad Capture formats. I recommend copying the Knowles library files to the UserLib directory. Default path to UserLib for Capture version 9.2 is: C:\Cadence\PSD\_14.2\tools\pspice\UserLib.

#### SCHEMATICS

##### ADDING A SYMBOL LIBRARY (.SLB)

1. Select *Editor Configuration...* from the *Options* menu to display the Editor Configuration dialog box.
2. Click on the *Library Settings* button to display the Library Settings dialog box.
3. There are two ways to add a new library to your list of global libraries:
  - (i) Type the library name including the path into the text box. Do not type the file extension .SLB.  
C:\MSim\_8\UserLib\library\_name or C:\MSim\_8\UserLib\folder\_name\library\_name
  - (ii) Click on the *Browse* button to locate the library file. Select the library file and click on the *Open* button.  
The library name and path will be displayed in the Library Settings dialog box.
4. Click on *Add\** to include the library in the list of global libraries that are available to all schematics designs. See the Orcad manuals for more information on local and global libraries.

Repeat steps 1-4 to install more symbol libraries.

##### ADDING A MODEL LIBRARY (.LIB)

1. Select *Library and Include Files..* from the *Analysis* menu to display the Library dialog box (Fig. C4).
  2. There are two ways to add a new model library:
    - (i) Type the library name including the path into the text box. Do not type the file extension .lib.  
C:\MSim\_8\UserLib\library\_name or C:\MSim\_8\UserLib\folder\_name\library\_name
    - (ii) Click on the *Browse* button to locate and open the library file in the UserLib folder. Select the library file and click on the *Open* button. The library name and path will be displayed in the Library dialog box.
  3. Click on *Add Library\** to include the library in the list of global libraries
- Repeat steps 1-3 to install more model libraries.

#### CAPTURE


The OLB file is the package file which contains the part graphic, pin definitions and properties. It defines the appearance of the part on the schematics page. The LIB file contains the .MODEL and the .SUBCKT statements. The LIB file is the PSpice model. It is the programming language that defines the part. If you see the part on your schematic but receive an error “Model \_\_MODEL or SUBCKT name\_\_ used by \_\_Part name\_\_ is undefined”, then Capture sees only the OLB package file. You must point the program to the LIB file by editing the PSPICE.INI file.

The next part of this section will instruct you on how to load the OLB files, edit Capture settings to locate the LIB files, and purge the Design Cache to ensure that all parts are the most current revisions without modifications. Unfortunately, it is easy to break the link between the part in design cache (on your schematic) and the library part in OLB/LIB libraries. The part on the schematic becomes a local instance and does not update when the library is


updated. I recommend reading the manual for more detailed information on Capture libraries: "Capture Users Guide Version 9.2.3" chapters 11 and 12 (file: capug.pdf).

### ADDING A SYMBOL (PACKAGE) LIBRARY (.OLB)

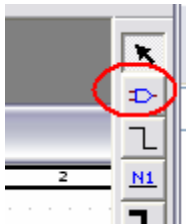1. Copy all library files (.OLB & .LIB) to your preferred directory.  
EXAMPLE: C:\Cadence\PSD\_14.2\tools\pspice\UserLib
2. Open any project file and then open the schematic page.
3. Click on the Place Part Icon



4. Select Add Library

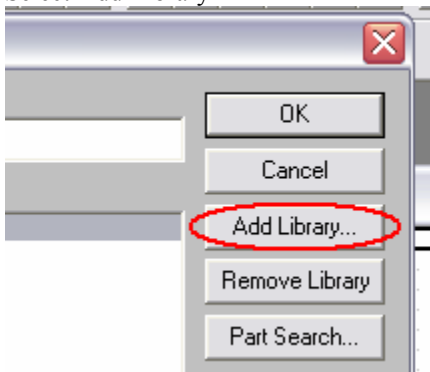

5. Locate the OLB library files, select the file and click the OPEN button
6. The library now appears in the Parts Browser. It will be available in all Project files (i.e., not just the open project but all project files).

### ADDING A MODEL LIBRARY (.LIB)

I prefer to edit the PSPICE.INI with a text editor. You may also be able to make these changes within the program. The most important lines are copied below. You should make changes to the path statements to match the file structure on your hard drive.

#### PSPICE.INI

Default file location = C:\Cadence\PSD\_14.2\tools\pspice

[PSPICE]

**LIBPATH="C:\Cadence\PSD\_14.2\tools\PSpice\UserLib";"C:\Cadence\PSD\_14.2\tools\PSpice\Library"**

*Make sure that the search path includes the directory containing the Knowles libraries as shown above.*

[PSPICE NETLIST]

**LINE1=.lib "nom.lib"**

**LINE2=**

*Many libraries may be listed in this section depending on your configuration. Add new libraries to the end of the list as shown below.*


**LINE3=.lib "C:\Cadence\PSD\_14.2\tools\pspice\UserLib\Knowles.lib"**

#### Update the Design Cache

You may already see parts from these libraries listed in the Design Cache. However, it is best to update your Project file to reference the original libraries. The Design Cache is not always current and can have outdated

versions of parts. In order to purge and update the cache, do the following:

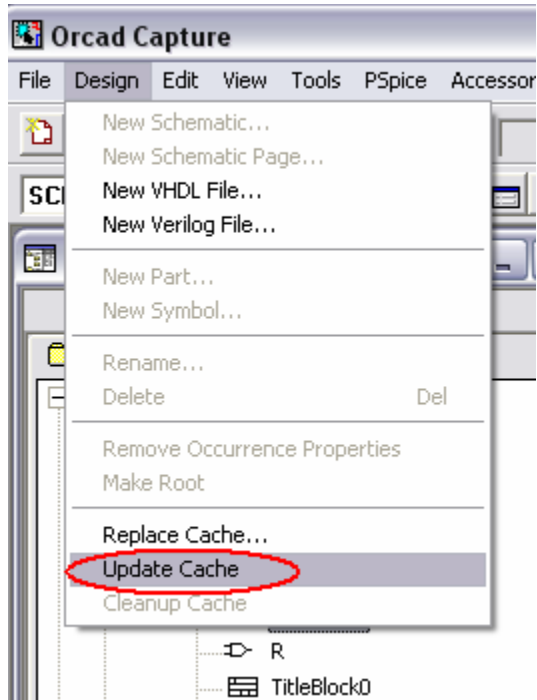1. Select the part or parts to update from the Design Cache list
2. Choose **Update Cache** from the Design menu to replace local instances of parts with the original library part. If **Update Cache** gives you an error message that it cannot find the library file then select **Replace Cache**.



# Appendix D

## Noise Simulations with Microphone Analogs

The circuit topology of microphone analogs was changed in Revision 6 to allow noise modeling. The newer analogs in Revision 6.1 and later (i.e., improved EM, FG and TM) will simulate acoustic and electrical noise.

### NOISE MODELING WITH SCHEMATICS OR CAPTURE

The “Noise Enabled” option must be selected in the simulation setup or profile. The sound source (enter VAC for I/V) and output node (enter 584 for Output Voltage) must also be identified to run a noise simulation. In the Probe window, Trace Expression VDB(584) will display the frequency response and Trace Expression DB(SQRT(NTOT(ONoise))) will display spectral noise.

### NOISE MODELING WITH NETLISTS

The module files (i.e., KEMxxx) can be used with any PSpice circuit simulation program. The netlist shown below is set up to simulate the response of the FG-3329 microphone and includes the following:

- FG-3329 analog (KEMFG1)
- .AC sweep between 100 Hz and 10 kHz (60 points per decade)
- .NOISE enabled where 584 is the output node and VK501 is the voltage source
- .PROBE enabled to create data file
- VK501 is the 74 dB SPL sound source with a -70 dB correction (i.e., unit conversion)

The 1 volt input is equivalent to 74 dB SPL. Since the analogs are in cgs units, the output voltage at node 584 requires a -70 dB correction to convert erg to Watt/sec (i.e.,  $V_{dB}(584) - 70$ ). Rather than subtracting 70 dB from the output, I prefer to scale the voltage source:  $VK501 = 1 \text{ volt} * 0.3162E-3$  where  $70 \text{ dB} = 0.3162E-3$ .

```
*=====
.AC DEC 60 100Hz 10kHz
VK501 581 0 AC .3162E-3
*=====
* KEMFG1
* FG-3329 standard FG (flat response)
* component values in SI units listed after the comment marker ";"

RK581      581 583 .600E+2 ; 6.00e+6
RK582      585 586 .660E+4 ; 6.60e+8
RK583      589 0 .100E+7 ; 1.00e+11
RK585      584 0 .220E+5 ; 2.20e+4

CK581      0 590 .250E-9 ; 2.50e-15
CK582      585 590 5.50E-9 ; 5.50e-14
CK583      587 588 2.23E-9 ; 2.23e-14
CK585      0 594 1.36E-12 ; 1.36e-12

LK581      583 590 .100E-1 ; 1.00e+3
LK582      586 587 .470E-1 ; 4.70e+3
LK583      585 589 .900 ; 9.00e+4

xTFMR1      588 0 594 0 TFMR PARAMS: PRI=1 SEC=111.854 ; 0.3537
M1          596 594 584 584 MOS_1
VK505      596 0 1.5

.SUBCKT TFMR 1 2 3 4 PARAMS:PRI=1 SEC=1
R1 1 2 9E+12
R3 3 4 9E+12
V1 1 5
G1 4 3 VALUE = {I(V1)*PRI/SEC}
E1 5 2 VALUE = {V(3,4)*PRI/SEC}
.ENDS

.MODEL MOS_1 NMOS
+ GAMMA=0.5 KP=61.85u L=3.6u LEVEL=1 VTO=-0.5 W=100u
+ RD=2.75k RS=2.75k RSH=30 NLEV=2 AF=0.8 KF=3E-25

*=====
.NOISE V(584) VK501
.PROBE
```



.END

\*=====

The netlist can be opened into a program such as Orcad PSpice and a simulation can be run which creates a data file. The results can be plotted in Orcad Probe<sup>TM</sup>. The sensitivity of the FG (i.e., dB V relative to 1 V/0.1 Pa) is given by  $V_{DB}(584)$  where node 584 is the electrical output node. Since I choose to scale the input voltage in this example, I do not need to subtract 70 dB from the output. **The spectral noise is given by  $DB(SQRT(NTOT(ONoise)))$ .** Noise modeling is available in only selected microphone analogs (see Appendix A).

## Appendix E

### Acoustical and Mechanical Analogs and Units

There are two types of analogs: mobility and impedance. In the impedance analog, mechanical force or sound pressure is equated with voltage and velocity or volume velocity is represented by current. In the mobility analog, the reverse is true. Voltage represents velocity and current equates force or pressure. Both methods produce equivalent results. We use the impedance analog to define equivalent circuit elements for the components in the Knowles microphones and receivers. Table E1 is a quick overview of the analogs and their units.

Electrical Quantity	Mechanical Analog	Mechanical Units	Mechanical Example	Acoustical Analog	Acoustical Units	Acoustical Example
Resistance <b>R</b> (Ohms)	Resistance <b>r<sub>m</sub></b>	$\text{gm} \cdot \text{sec}^{-1}$	Drag in a viscous fluid or damping	Resistance <b>R<sub>A</sub></b>	$\text{gm} \cdot \text{cm}^{-4} \cdot \text{sec}^{-1}$	Air flow through a screen
Inductance <b>L</b> (Henries)	Mass <b>m</b>	gm	Mass	Inertance <b>M</b>	$\text{gm} \cdot \text{cm}^{-4}$	Air in a tube
Capacitance <b>C</b> (Farads)	Compliance <b>c<sub>m</sub></b>	$\text{sec}^2 \cdot \text{gm}^{-1}$	Spring	Compliance <b>C<sub>A</sub></b>	$\text{gm}^{-1} \cdot \text{cm}^4 \cdot \text{sec}^2$	Air in a cavity
Voltage <b>V</b> (Volts)	Force <b>F</b>	$\text{gm} \cdot \text{cm} \cdot \text{sec}^{-2}$		Pressure <b>P</b>	$\text{gm} \cdot \text{cm}^{-1} \cdot \text{sec}^{-2}$	
Current <b>i</b> (Amperes)	Velocity <b>v</b>	$\text{cm} \cdot \text{sec}^{-1}$		Volume velocity <b>u</b>	$\text{cm}^3 \cdot \text{sec}^{-1}$	

**Table E1:** Acoustical and mechanical quantities and their electrical analogs.

# Appendix F


## Netlist Modules and Library Subcircuits

Electrical Analogs for Knowles Electronics Transducers are designed to be used with a PSpice circuit analysis program. The library files (\*.LIB) are text files containing subcircuit definitions of over 300 transducers. These subcircuits use the standard PSpice format. Even if you are not using the Orcad circuit simulator, you may find these files helpful for your own circuit program. This section contains detailed information on node numbers and device specifications for using these analogs in your models.

### Node Numbering, Device Specifications, & Modules

The electrical analogs observe the same constraints as previously released models (described in reports 10531-1 and 10531-2). The constraints for node numbers and for device specifications are:

- All device and node numbers are in the range 400 to 699.
- To distinguish parts of these analog modules from others in your application, all device specifications have the letter 'K' after the reserved device specifying letter. That is, all capacitor devices in the analog have a designation such as CK5xx.
- The programs are grouped by functional modules. Each module has a generic name and a serial identification. The block diagrams in Fig. F1. show the layout of nodes for attachment to the program modules that are provided.

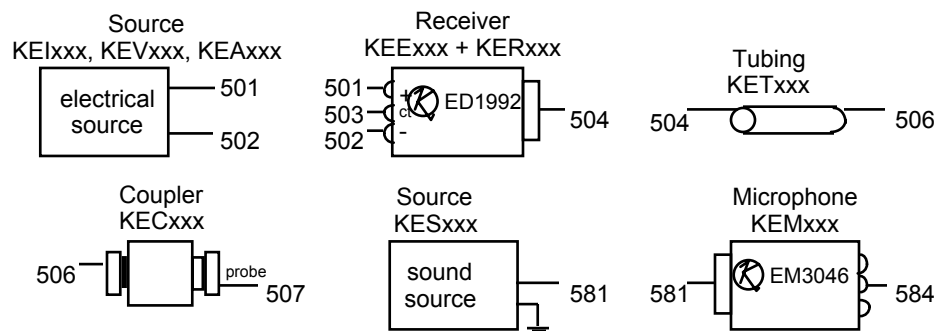

**FIG. F1:** Module names and terminating node numbers for the transducer analogs.

### Receiver Modules, Node Numbers and Subcircuits

PSpice receiver simulation must contain the appropriate combination of KEExxx and KERxxx modules. The generic module names are listed below followed by xxx to indicate the three-digit serial number. Appendix A. has a list of all available transducer models and their associated modules (i.e., module name + serial number).

#### Module Name Description

KEExxx	electrical parameters of a particular receiver
KERxxx	basic transducer construction
KETxxx	acoustic transmission paths
KECxxx	standard test couplers
KEFxxx	program termination modules: KEF001 enables .PROBE and exits the program and KEF002 exits the program.

Three types of receiver input modules are included. They set up an AC analysis from 100 Hz to 10 kHz with 100 points per decade.

KEIxxx	provide input conditions to simulate the constant current conditions such as an amplifier with high output impedance. They represent values frequently found on Knowles product specifications, Sheet 2.1. The three digits specify the hundredth's of rms milliamperes (e.g., KEI033 = 0.33 mA AC constant current source).
KEVxxx	provide input conditions to simulate the constant voltage conditions such as an amplifier with low output impedance. They are also appropriate for the amplified versions of receiver transducers. They represent values frequently found on Knowles product specifications, Sheet 2.1. The three digits specify the hundredth's of rms volts (e.g., KEV100 = 1.00 volt AC constant voltage source).
KEAxxx	provides input conditions to simulate the maximum available power conditions (MAP) such as an amplifier with finite output impedance and is not limited by other considerations. The maximum power available from these sources is 1 mW. They represent values found on Knowles product specifications, Sheet 2.1. The three digits specify the source impedance in tens of ohms.

All Knowles electrical analogs are restricted to node numbers in the range 400 to 699. Specific node numbers are reserved for terminating each module and joining modules.

- 501 the positive electrical terminal in any KEExxx module.
- 502 the negative electrical terminal in any KEExxx module.
- 503 the center-tap of any three terminal receiver represented by a KEExxx module. While the node will always be present, it should only be used when the device being examined has three terminals.

For Knowles amplified receivers (i.e., EP and ES), node 503 provides a access point where power supply feedback can be introduced. As the program is supplied, a 0.0 volt D.C. source (VK502) is connected to this node to satisfy program requirements.

- 504 the acoustical terminal of any KERxxx module. It will also be the node number of the input end of any KETxxx acoustical transmission line.
- 505 joins the KEExxx and KERxxx modules. No other interpretation should be attached to the function of this node.
- 506 the output terminal of any KETxxx transmission path module and the input terminal of any KECxxx coupler module.
- 507 the output terminal of any KECxxx coupler module. It will yield the sound pressure at the microphone in the coupler.

**When the input is in terms of volts and amperes the output energy is in terms of watt-seconds. To convert a node voltage to dB SPL you must add 144 dB.** The usual query would be DB(V(507))+144 (or DBV(507)+144) for the SPL in a coupler. (70 dB of this factor is to change from a watt-second to an erg reference frame and 74 dB to change from dynes/cm<sup>2</sup> to 0.0002 dynes/cm<sup>2</sup> which is the 0 dB SPL reference level.). The 70dB factor is a consequence of using cgs units for acoustical and mechanical analogs (i.e., centimeter-gram-second unit system).

A receiver requires two module files KEExxx and KERxxx. This allows many combinations of coils and damping within one series of receivers (see Appendix A). The library files (\*.LIB) define all of the module files as subcircuits. The library format has changed from Rev 6 making it easier to create new analogs with existing modules files and to make updates. The \*.SLB library file contains the part symbol, pin attributes, and links the symbol to the subcircuits.

Receiver subcircuit:

```
.SUBCKT ED1913 501 502 504
xKEE 501 502 503 505 KEEED1
xKER 505 504 KERED1
.ENDS
```

#### Microphone Modules, Node Numbers and Subcircuits

The circuit topology of the microphone analog has been changed from the original topology used in previous releases (i.e., Release 1 through 5). This change was necessary to provide the option for noise modeling which is available for some selected analogs (see Appendices A). The microphone modules have the designation KEMxxx and utilize the node numbers between 581 and 599. The device designations follow the convention used for receivers. All Knowles microphones are active devices. No attempt has been made to simulate the D.C. voltage levels. There is no substantial bidirectional interaction between the acoustical and electrical portions of the analog. KESxxx modules are supplied to apply a frequency independent sound pressure to input node of the microphone (i.e., node 581). The three digits xxx are the sound pressure in SPL. Modules are supplied for 50, 55, 60, 65, 70, 74 and 90 SPL.

The applied voltage is numerically equal to the applied sound pressure in dynes/cm<sup>2</sup> (i.e., 1 volt is equivalent to 74dB SPL). The electrical output signal is volts and /or amperes. **70 dB must be subtracted from the output voltage** or scale the input voltage by -70dB (i.e., scale sound source by 1/3162). The 70 dB of this factor is to change from a watt-second to an erg reference frame. The sound pressure is referenced to node 0 (i.e., ground). The electrical output signal is also referenced to node 0.

The new analogs observe the same constraints for node numbers and for device specifications as previously released modules.

581 the principal acoustical terminal. The electrical signal applied here is to be numerically equal to the applied sound pressure in dynes/cm<sup>2</sup> (i.e., 1 volt is equivalent to 74 dB SPL).

584 the electrical output node. The signal will be in volts and/or amperes.

VK581 is a dummy voltage source connected to node 595. It is included to provide a place to insert power supply fluctuations either through redefining it as an A.C. source or deleting it and inserting the power supply signal on node 585.